



**Programa Doutoral - Tópicos Avançados em Electrónica (TAE)
(Advanced Topics in Electronics)**

Exam 10/11 (5 pages)

1- CMOS technology

1.1 Currently, what is the most used integrated circuit technology in the world?

Select only one answer:

- a) Bipolar technology
- b) BiCMOS technology
- c) GaAs technology
- d) CMOS technology
- e) None of the above

| |
|--------------------------|
| <input type="checkbox"/> |

1.2 Select the statement that is true from the ones below:

Select only one answer:

- a) The power dissipation in digital CMOS circuits is inversely proportional to the square of the transistor channel length
- b) The gate leakage current in a CMOS technology with transistors with a smaller channel length is smaller than in a CMOS technology with transistors with a larger one.
- c) A MOS transistor with a smaller threshold voltage value has larger leakage current than a transistor with a larger threshold voltage value.
- d) The gate capacitance of a MOS transistor in the linear region is smaller than the gate capacitance of a MOS transistor in the saturation region.
- e) None of the above.

| |
|--------------------------|
| <input type="checkbox"/> |

1.3 Increasing the drain current in a MOS transistor results in:

Select only one answer:

- a) a smaller V_{DSsat} voltage
- b) a larger DC gain of the device (gm/gds)
- c) a larger transition frequency (gm/Cgs)
- d) a smaller output noise
- e) None of the above.

| |
|--------------------------|
| <input type="checkbox"/> |

1.3 What noise source does not exist in a MOS transistor?

Select only one answer:

- a) Thermal noise
- b) Flicker noise
- c) Shot noise
- d) All of the above

| |
|--------------------------|
| <input type="checkbox"/> |
| <input type="checkbox"/> |
| <input type="checkbox"/> |
| <input type="checkbox"/> |

2- Advanced Amplifier Topologies

2.1 In cascoded topologies of Operational Transconductance Amplifiers (OTAs), such as the folded-cascoded or the telescopic cascoded OTA, the expression for the GBW includes:

Select only one answer:

- a) The gm of the cascode devices
- b) The gm of the common-source input devices used in the differential pair
- c) The gds of the cascode devices
- d) All of the above
- e) None of the above.

| |
|--|
| |
| |
| |
| |
| |

2.2 In Miller-Compensated Two-stage OTAs, when we increase the value of the load capacitor (C_L) above a certain limit, the amplifier:

Select only one answer:

- a) becomes more stable
- b) becomes unstable
- c) has a decrease in the DC gain
- d) has an increase in the DC gain
- e) None of the above.

| |
|--|
| |
| |
| |
| |
| |

2.3 In a folded-cascoded OTAs if we double the DC biasing current in all devices (NMOS and PMOS):

Select only one answer:

- a) The gain increases by 6 dB
- b) The gain increases by 3 dB
- c) The gain decreases by 6 dB
- d) The gain decreases by 3 dB
- e) None of the above

| |
|--|
| |
| |
| |
| |
| |

2.4 In two-stage Miller-compensated OTAs, the ways to increase the GBW are:

Select only one answer:

- a) increase the bias current of the devices used in the differential pair
- b) reduce the compensation capacitance, C_c
- c) reduce the V_{DSsat} of the devices used in the differential pair
- d) All of the above
- e) None of the above

| |
|--|
| |
| |
| |
| |
| |

| |
|----------------|
| 3- LNAs |
|----------------|

3.1 Consider that the 1dB compression point at the output of a LNA is -20 dBm and its output dynamic range is 20 dB. Determine the minimum input signal power detectable by the LNA knowing that its power gain is 20 dB.

- a) -40 dBm
- b) -60 dBm
- c) -80 dBm
- d) -20 dBm
- e) None of the above.

Select only one answer:

| |
|--|
| |
| |
| |
| |
| |

3.2 Figure 1 shows the input part of an integrated LNA in 130 nm technology for RF narrowband applications. The component L_s represents the inductance of the bonding wire which has approximately a 1 nH value. Calculate the value of transistor transition frequency ($f_T = g_m/C_{gs}$) needed to achieve a 50 Ω (real part) matching at the input ($Z_{in}=1/Y_{in}$) in resonance.

 


Figure 1 – LNA input.

(Suggestion: neglect the output transistor conductance g_{ds} and drain-gate capacitance C_{dg} in the simplified AC transistor model.)

- a) 100×10^9 Hz (100 GHz)
- b) 5×10^9 Hz (5 GHz)
- c) 5×10^{10} Hz (50 GHz)
- d) 20×10^9 Hz (20 GHz)
- e) None of the above.

Select only one answer:

| |
|--|
| |
| |
| |
| |
| |

3.3 In order to fully integrate a 600 MHz RF direct-conversion receiver in CMOS technology, the designer of the LNA and the following Mixer circuit should attend that:

- a) is mandatory to include 50 Ω matching network between the two blocks.
- b) is mandatory to include 75 Ω matching network between the two blocks.
- c) the 50 Ω matching is not necessary since the distributed effects between the two blocks can be neglected and the signal is treated as a voltage one.
- d) the 50 Ω matching is not necessary due to the low input impedance associated to the MOS transistor gate at low frequencies.
- e) None of the above

Select only one answer:

| |
|--|
| |
| |
| |
| |
| |
| |

4- Oscillators and Mixers

4.1- Accurate quadrature oscillators are required in low-IF receivers for:

Select only one answer:

- a) Image rejection without external filtering.
- b) RF signal isolation.
- c) RF signal amplification.
- d) Converting the RF signal for the IF frequency.
- e) None of the above.

| |
|--------------------------|
| <input type="checkbox"/> |

4.2- The Barkhausen criteria is used in oscillator design:

Select only one answer:

- a) Only in linear oscillators.
- b) Only in nonlinear oscillators.
- c) In all type of oscillators.
- d) Only in square signal oscillators.
- e) None of the above.

| |
|--------------------------|
| <input type="checkbox"/> |

4.3- The main advantage of the RC oscillator over the LC oscillator is:

Select only one answer:

- a) Less phase noise.
- b) Lower power consumption.
- c) Occupies less chip area and do not need RF options.
- d) Less harmonic distortion
- e) None of the above

| |
|--------------------------|
| <input type="checkbox"/> |

4.4- The Gilbert Cell is a mixer of type:

Select only one answer:

- a) passive.
- b) passive with parametric amplification.
- c) active single-balanced.
- d) active double balanced.
- e) None of the above.

| |
|--------------------------|
| <input type="checkbox"/> |

5 - CAD Tools

5.1 – In the presented optimization platform (ngEDA), the “chromosome” file includes:

Select only one answer:

- a) The range values for the circuit variables, i.e., design space (e.g. width and length of transistors);
- b) The circuit indicators to be achieved;
- c) The fabrication technology parameters;
- d) All previous values;
- e) None;

| |
|--|
| |
| |
| |
| |
| |

5.2 – The transistor’s models used in the simulation/optimization phase allow:

Select only one answer:

- a) Calculate the circuit performance;
- b) Compute the transient and dc I-V (current-voltage) characteristics; the parasitic elements (capacitances, resistances, inductances);
- c) All previous;
- d) None of the above;

| |
|--|
| |
| |
| |
| |

5.3- The design rules check (DRC) tools are to:

Select only one answer:

- a) Verify the layout conformance against the foundry fabrication rules;
- b) Verify the layout conformance against the circuit netlist;
- c) Verify if the size of the elements (in layout) meet the circuit specifications
- d) None of the above;

| |
|--|
| |
| |
| |
| |

NAME:

Ph. D. Student #: